 


Tp6 : Modélisation de machines à états finis

Exercice 1 :

1)



2)

Moore.vhdl

```

32 entity moore is
33 Port (
34     clk    : in  STD_LOGIC;
35     reset  : in  STD_LOGIC;
36     E      : in  STD_LOGIC;
37     S      : out STD_LOGIC
38 );
39 end moore;
40
41 architecture Behavioral of moore is
42     type Etat_Type is (Etat0, Etat1, Etat2, Etat3);
43     signal Etat_present, Etat_futur : Etat_Type := Etat0;
44 begin
45     process(clk, reset)
46     begin
47         if reset = '0' then
48             Etat_present <= Etat0;
49         elsif rising_edge(clk) then
50             Etat_present <= Etat_futur;
51         end if;
52     end process;
53
54     process(E, Etat_present)
55     begin
56         case Etat_present is
57             when Etat0 =>

```

```

58         when Etat0 =>
59             if E = '1' then
60                 Etat_futur <= Etat1;
61             else
62                 Etat_futur <= Etat0;
63             end if;
64         when Etat1 =>
65             if E = '1' then
66                 Etat_futur <= Etat2;
67             else
68                 Etat_futur <= Etat0;
69             end if;
70         when Etat2 =>
71             if E = '1' then
72                 Etat_futur <= Etat3;
73             else
74                 Etat_futur <= Etat0;
75             end if;
76         when Etat3 =>
77             if E = '1' then
78                 Etat_futur <= Etat3;
79             else
80                 Etat_futur <= Etat0;
81             end if;
82         end case;
83     end process;
84
85 process(Etat_present)
86     begin
87         case Etat_present is
88             when Etat3 =>
89                 S <= '1';
90             when others =>
91                 S <= '0';
92             end case;
93         end process;
94     end Behavioral;
95
96

```

Mealy.vhdl

```
41 architecture Behavioral of mealy is
42     type Etat_Type is (Etat0, Etat1, Etat2);
43     signal Etat_present, Etat_futur : Etat_Type := Etat0;
44 begin
45     process(clk, reset)
46     begin
47         if reset = '0' then
48             Etat_present <= Etat0;
49         elsif rising_edge(clk) then
50             Etat_present <= Etat_futur;
51         end if;
52     end process;
53
54     process(E, Etat_present)
55     begin
56         S <= '0';
57         case Etat_present is
58             when Etat0 =>
59                 if E = '1' then
60                     Etat_futur <= Etat1;
61                 else
62                     Etat_futur <= Etat0;
63                 end if;
64             when Etat1 =>
65                 if E = '1' then
66                     Etat_futur <= Etat2;
67                 else
68                     Etat_futur <= Etat0;
69                 end if;
70             when Etat2 =>
71                 if E = '1' then
72                     Etat_futur <= Etat2;
73                     S <= '1';
74                 else
75                     Etat_futur <= Etat0;
76                 end if;
77         end case;
78     end process;
79
80 end Behavioral;
```

3) Test Bench :

Tb_moore.vhdl

```

process
begin
    -- Réinitialisation
    reset <= '0';
    wait for 20 ns;
    reset <= '1';
    wait for 20 ns;

    E <= '0'; wait for CLK_PERIOD;
    E <= '1'; wait for CLK_PERIOD;
    E <= '1'; wait for CLK_PERIOD;
    E <= '1'; wait for CLK_PERIOD;
    E <= '0'; wait for CLK_PERIOD;

    E <= '1'; wait for CLK_PERIOD;
    E <= '0'; wait for CLK_PERIOD;
    E <= '1'; wait for CLK_PERIOD;
    E <= '1'; wait for CLK_PERIOD;

    wait;
end process;
end behavior;

```

The screenshot shows a simulation environment with a table of simulation objects for 'tb_moore' and a corresponding timing diagram. The table lists the following objects:

Object Name	Value
clk	1
reset	1
e	1
s	1
clk_period	10000 ps


The timing diagram shows the waveforms for these signals over time. The 'clk' signal is a periodic square wave. The 'reset' signal starts at 0 and transitions to 1 at approximately 382 ms. The 'e' signal transitions from 0 to 1 at approximately 384 ms. The 'clk_period' signal is a constant value of 10000 ps.

Tb_mealy.vhdl

```

82
83     process
84     begin
85         -- Réinitialisation
86         reset <= '0';
87         wait for 20 ns;
88         reset <= '1';
89         wait for 20 ns;
90
91         E <= '0'; wait for CLK_PERIOD;
92         E <= '1'; wait for CLK_PERIOD;
93         E <= '1'; wait for CLK_PERIOD;
94         E <= '1'; wait for CLK_PERIOD;
95         E <= '0'; wait for CLK_PERIOD;
96
97         E <= '1'; wait for CLK_PERIOD;
98         E <= '0'; wait for CLK_PERIOD;
99         E <= '1'; wait for CLK_PERIOD;
100        E <= '1'; wait for CLK_PERIOD;
101
102        wait;
103    end process;
104 END;


```

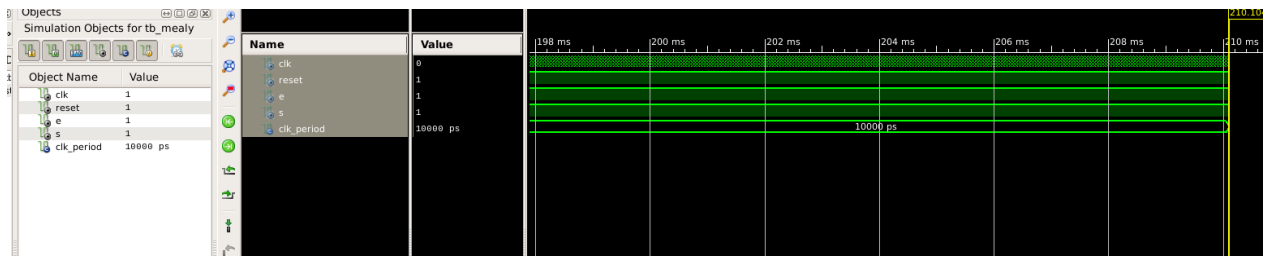

- 4) Les sorties d'une machine de Mealy dépendent des entrées et changent immédiatement (asynchrone), tandis que celles d'une machine de Moore dépendent uniquement de l'état présent et changent sur un front d'horloge (synchrone).

Exercice 2 :

1)

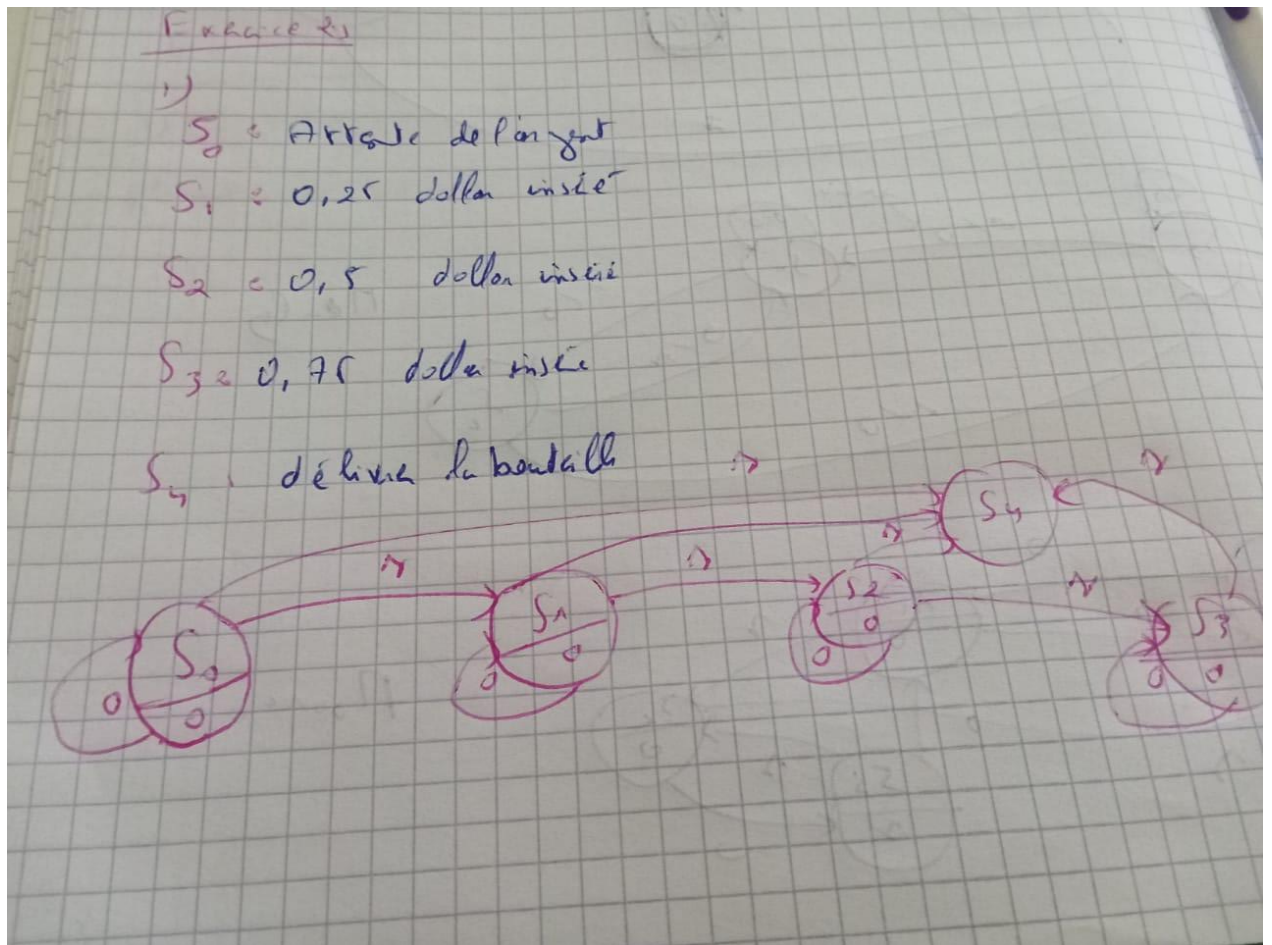

2)

Moore.vhdl

```


32 entity moore is
33     Port (
34         clk          : in  STD_LOGIC;
35         reset        : in  STD_LOGIC;
36         D_in         : in  STD_LOGIC;
37         Q_in         : in  STD_LOGIC;
38         dispense     : out STD_LOGIC;
39         change       : out STD_LOGIC
40     );
41 end moore;
42
43 architecture Behavioral of moore is
44     type state_type is (IDLE, Q25, Q50, Q75, dis);
45     signal current_state, next_state : state_type := IDLE;
46
47     signal internal_dispense : STD_LOGIC := '0';
48     signal internal_change   : STD_LOGIC := '0';
49
50 begin
51     internal_dispense <= '1';
52     dispense <= internal_dispense;
53
54
55
56
57
58
59
60
61
62
63
64
65
66
67
68
69
70
71

```

```

72         case current_state is
73             when IDLE =>
74                 if D_in = '1' then
75                     next_state <= dis;
76                 elsif Q_in = '1' then
77                     next_state <= Q25;
78                 end if;
79
80             when Q25 =>
81                 if D_in = '1' then
82                     next_state <= dis;
83                 elsif Q_in = '1' then
84                     next_state <= Q50;
85                 end if;
86
87             when Q50 =>
88                 if D_in = '1' then
89                     next_state <= dis;
90                 elsif Q_in = '1' then
91                     next_state <= Q75;
92                 end if;
93
94             when Q75 =>
95                 if D_in = '1' then
96                     next_state <= dis;
97                 end if;
98             -----,
99
100             when dis =>
101                 internal_dispense <= '1';
102                 internal_change   <= '1';
103                 next_state        <= IDLE;
104
105             when others =>
106                 next_state <= IDLE;
107         end case;
108     end process;
109
110 end Behavioral;
111
112

```

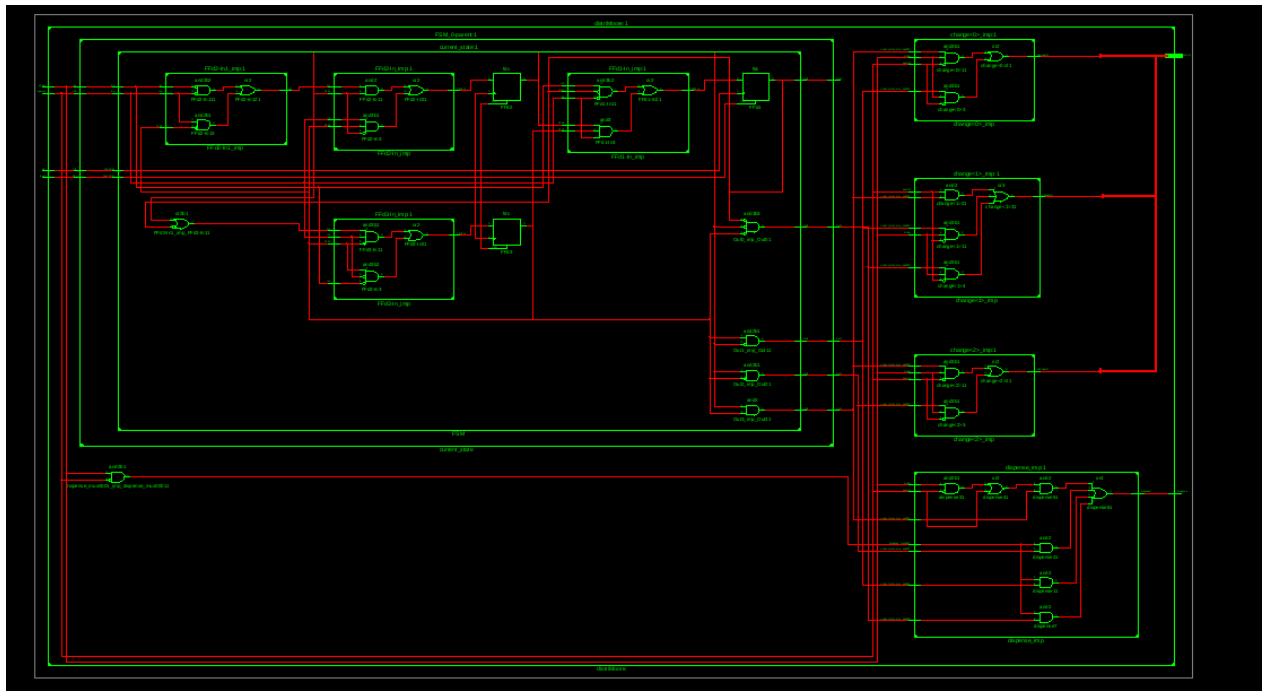




3) Test Bench :


```

86
87     stimulus: process
88 begin
89     reset <= '1';
90     wait for 20 ns;
91     reset <= '0';
92
93     Q_in <= '1';
94     wait for 20 ns;
95     Q_in <= '0';
96     wait for 20 ns;
97
98     Q_in <= '1';
99     wait for 20 ns;
100    Q_in <= '0';
101    wait for 20 ns;
102
103    D_in <= '1';
104    wait for 20 ns;
105    D_in <= '0';
106
107    wait;
108 end process;
109
110
111
112
113 END;


```

 

  

Exercise 3 :

1)

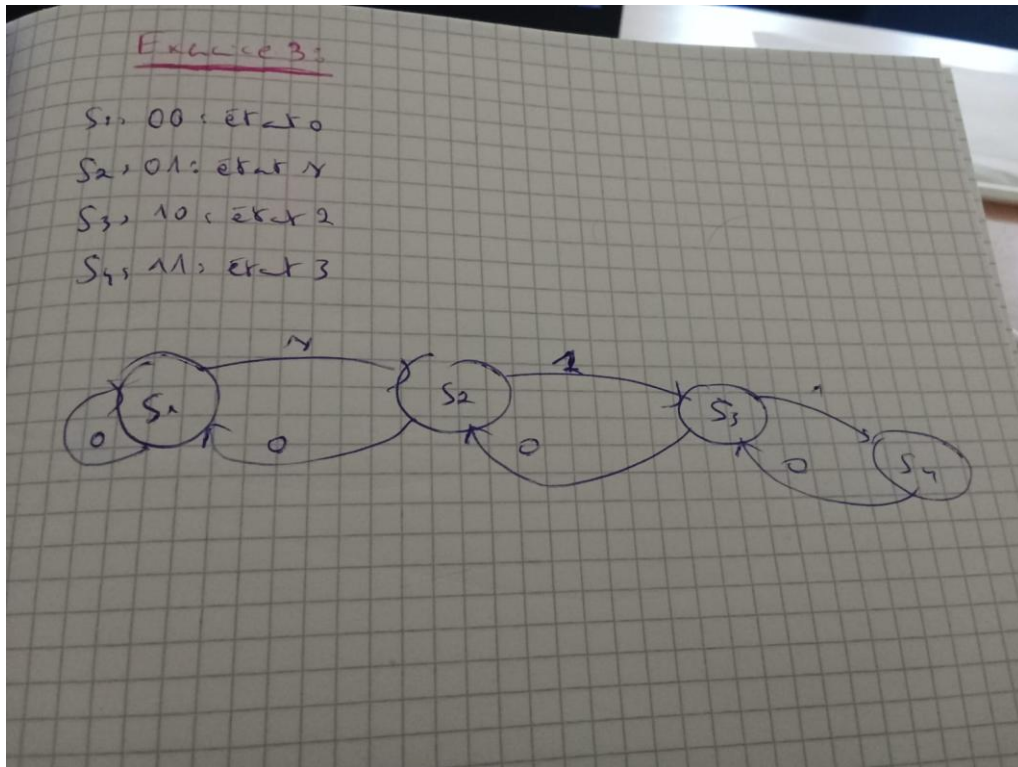

2)

```

6  entity moore is
7  Port (
8      clk      : in  STD_LOGIC;
9      reset    : in  STD_LOGIC;
10     up       : in  STD_LOGIC;
11     cnt      : out STD_LOGIC_VECTOR(1 downto 0)
12 );
13 end moore;
14
15
16 architecture Behavioral of moore is
17     signal count : STD_LOGIC_VECTOR(1 downto 0) := "00";
18     signal count_int : unsigned(1 downto 0);
19     begin
20         count_int <= unsigned(count);
21         process(clk, reset)
22         begin
23             if reset = '1' then
24                 count_int <= (others => '0');
25             elsif rising_edge(clk) then
26                 if up = '1' then
27                     count_int <= count_int + 1;
28                 else
29                     count_int <= count_int - 1;
30                 end if;
31             end if;
32         end process;
33         cnt <= std_logic_vector(count_int);
34     end Behavioral;

```

3) Test Bench :

```
78
79 stimulus: process
80   begin
81     reset <= '1';
82     wait for 20 ns;
83     reset <= '0';
84     wait for 20 ns;
85
86     up <= '1';
87     wait for 40 ns;
88     up <= '0';
89     wait for 40 ns;
90
91     up <= '0';
92     wait for 40 ns;
93     up <= '1';
94     wait for 40 ns;
95
96     up <= '1';
97     wait for 40 ns;
98     up <= '0';
99     wait for 40 ns;
100
101   wait;
102 end process;
103
104 END;
```

