

Tp5 : Modélisation Séquentielle


Stockage et registre

Exercice 1 :

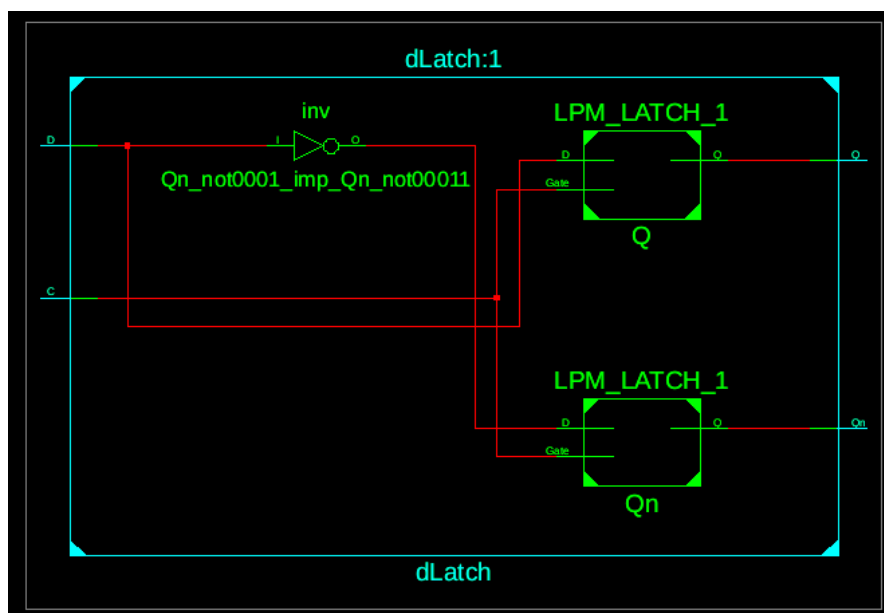1) Modèle VHDL modélisant les types de bascule D et test bench :


D_Latch

```
32 entity dLatch is
33     Port ( C : in  STD_LOGIC;
34           D : in  STD_LOGIC;
35           Q : out STD_LOGIC;
36           Qn : out STD_LOGIC);
37 end dLatch;
38
39 architecture Behavioral of dLatch is
40
41 begin
42     process (D,C)
43     begin
44         if C = '1' then
45             Q <= D;
46             QN <= not D;
47         end if;
48     end process;
49
50 end Behavioral;
51
52
```



Test bench pour D_lach:

```
34 ENTITY Dlach_tb IS
35 END Dlach_tb;
36
37 ARCHITECTURE behavior OF Dlach_tb IS
38
39     -- Component Declaration for the Unit Under Test (UUT)
40
41     COMPONENT dLatch
42     PORT(
43         C : IN  std_logic;
44         D : IN  std_logic;
45         Q : OUT std_logic;
46         Qn : OUT std_logic
47     );
48     END COMPONENT;
49
50
51
52     --Inputs
53     signal C : std_logic := '0';
54     signal D : std_logic := '0';
55
56     --Outputs
57     signal Q : std_logic;
58     signal Qn : std_logic;
59
60
61 BEGIN
62
63     -- Instantiate the Unit Under Test (UUT)
64     uut: dLatch PORT MAP (
65         C => C,
66         D => D,
67         Q => Q,
68         Qn => Qn
69     );
70
71
72     process
73     begin
74         D<= '0'; C <= '0'; wait for 10 ns;
75         D <= '1'; wait for 10 ns;
76
77         C <= '1'; wait for 10 ns;
78         D <= '0'; wait for 10 ns;
79         D <= '1'; wait for 10 ns;
80
81         C <= '0'; wait for 10 ns;
82         D <= '0'; wait for 10 ns;
83
84         wait;
85     end process;
86
87 END;
```

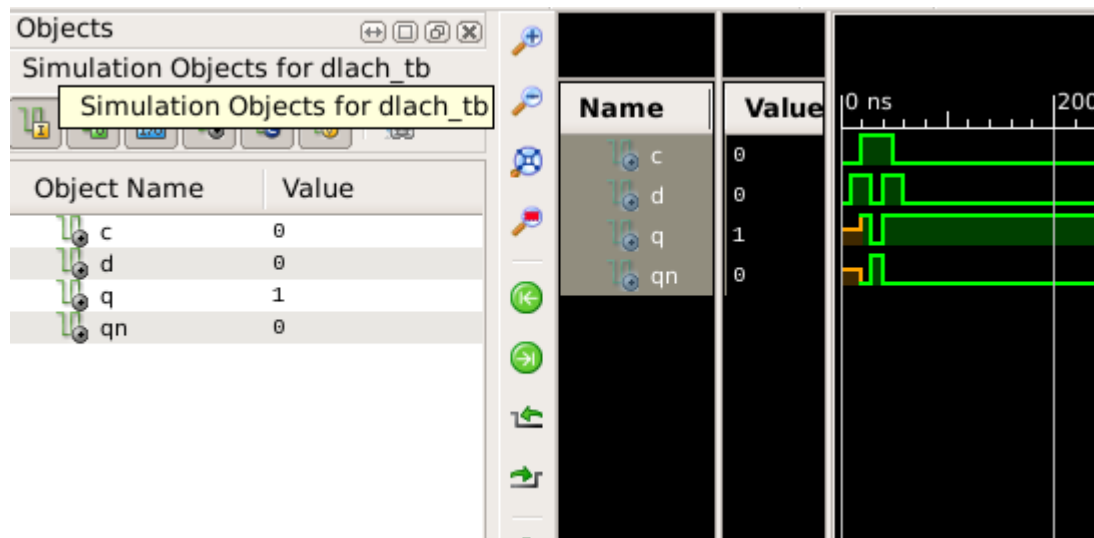

D_Flip_Flop


```

31
32 entity dFlipFlop is
33     Port ( Clk : in  STD_LOGIC;
34           D : in  STD_LOGIC;
35           Q : out  STD_LOGIC;
36           Qn : out  STD_LOGIC);
37 end dFlipFlop;
38
39 architecture Behavioral of dFlipFlop is
40
41 begin
42     process (Clk)
43     begin
44         if rising_edge(Clk) then
45             Q <= D;
46             Qn <= not D;
47         end if;
48     end process;
49
50 end Behavioral;
51

```

Testbench pour D_Flip_Flop:

```
71   Clk_Process: process
72   begin
73       Clk <= '0';
74       wait for 10 ns;
75       Clk <= '1';
76       wait for 10 ns;
77   end process;
78
79   Stimulus : process
80   begin
81       D <= '0'; wait for 25 ns;
82       D <= '1'; wait for 20 ns;
83       D <= '0'; wait for 20 ns;
84       D <= '1'; wait for 20 ns;
85       D <= '0'; wait for 20 ns;
86       D <= '1'; wait for 20 ns;
87       D <= '0'; wait for 20 ns;
88       D <= '1'; wait for 20 ns;
89       D <= '0'; wait for 20 ns;
90       D <= '1'; wait for 20 ns;
91       D <= '0'; wait for 20 ns;
92       D <= '1'; wait for 20 ns;
93   wait;
94
95   end process;
96
97 END;
```

 

D_Flip_Flop avec réinitialisations asynchrones

```
2 entity DflipFlopReinAsync is
3     Port ( R : in  STD_LOGIC;
4           Clk : in  STD_LOGIC;
5           D : in  STD_LOGIC;
6           Q : out  STD_LOGIC;
7           Qn : out  STD_LOGIC);
8 end DflipFlopReinAsync;
9
10 architecture Behavioral of DflipFlopReinAsync is
11
12 begin
13 process (R, Clk)
14     begin
15         if R = '0' then
16             Q <= '0';
17             Qn <= '1';
18
19             elsif rising_edge(Clk) then
20                 Q <= D;
21                 Qn <= not D;
22             end if;
23         end process;
24
25 end Behavioral;
```

Test Bench pour D_Flip_Flop avec réinitialisations asynchrones

```
--Inputs
signal R : std_logic := '1';
signal Clk : std_logic := '0';
signal D : std_logic := '0';


--Outputs
signal Q : std_logic;
signal Qn : std_logic;

-- Clock period definitions
constant Clk_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
ut: DflipFlopReinAsync PORT MAP (
    R => R,
    Clk => Clk,
    D => D,
    Q => Q,
    Qn => Qn
);
```

```
76 Clk_process :process
77 begin
78     Clk <= '0';
79     wait for Clk_period/2;
80     Clk <= '1';
81     wait for Clk_period/2;
82 end process;
83
84 stim_proc: process
85 begin
86     R <= '0';
87     wait for 20 ns;
88
89     R <= '1';
90     D <= '0';
91     wait for clk_period * 2;
92
93     D <= '1';
94     wait for clk_period * 2;
95
96     D <= '0';
97     wait for clk_period / 2;
98
99     R <= '0';
100     wait for clk_period;
101     wait;
102 end process;
103
104
105 END;
```

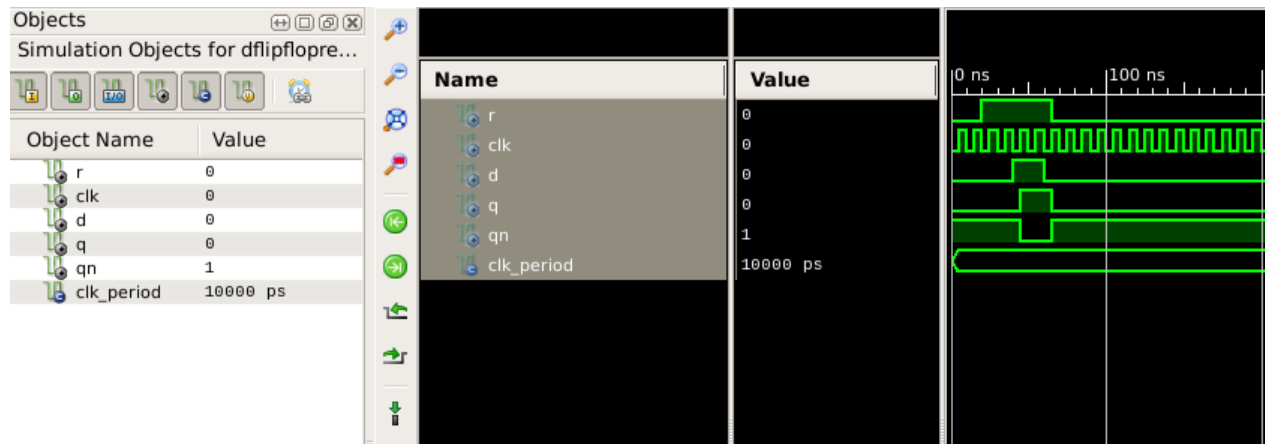

D_Flip_Flop avec Asynchrones Reset and Preset

```

31
32 entity dFlipFlopAsync is
33     Port ( R : in  STD_LOGIC;
34           P : in  STD_LOGIC;
35           Clk : in  STD_LOGIC;
36           D : in  STD_LOGIC;
37           Q : out STD_LOGIC;
38           Qn : out STD_LOGIC);
39 end dFlipFlopAsync;
40
41 architecture Behavioral of dFlipFlopAsync is
42
43 begin
44 process (R, P, Clk)
45     begin
46         if (R = '0') then
47             Q <= '0';
48             Qn <= '1';
49
50         elsif (P = '0') then
51             Q <= '1';
52             Qn <= '0';
53
54         elsif rising_edge(Clk) then
55             Q <= D;
56             Qn <= NOT D;
57         end if;
58     end process;
59
60 end Behavioral;
61
62

```

Test bench pour D_Flip_Flop avec Asynchrones Reset and Preset

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: dFlipFlopAsync PORT MAP (
```

```
    R => R,
```

```
    P => P,
```

```
    Clk => Clk,
```

```
    D => D,
```

```
    Q => Q,
```

```
    Qn => Qn
```

```
);
```

```
process
```

```
begin
```

```
    while true loop
```

```
        Clk <= '0';
```

```
        wait for 10 ns;
```

```
        Clk <= '1';
```

```
        wait for 10 ns;
```

```
    end loop;
```

```
end process;
```

```
88
```

```
89     process
```

```
90     begin
```

```
91         R <= '1'; P <= '1'; D <= '0'; wait for 20 ns;
```

```
92
```

```
93         R <= '0'; P <= '1'; wait for 20 ns;
```

```
94         R <= '1'; wait for 20 ns;
```

```
95
```

```
96         R <= '1'; P <= '0'; wait for 20 ns;
```

```
97         P <= '1'; wait for 20 ns;
```

```
98
```

```
99         R <= '1'; P <= '1'; D <= '1'; wait for 30 ns;
```

```
100
```

```
101         wait for 10 ns;
```

```
102         D <= '0'; wait for 20 ns;
```

```
103
```

```
104         D <= '1'; wait for 20 ns;
```

```
105
```


```
106         wait;
```

```
107     end process;
```

```
108
```

```
109 END;
```

```
110
```

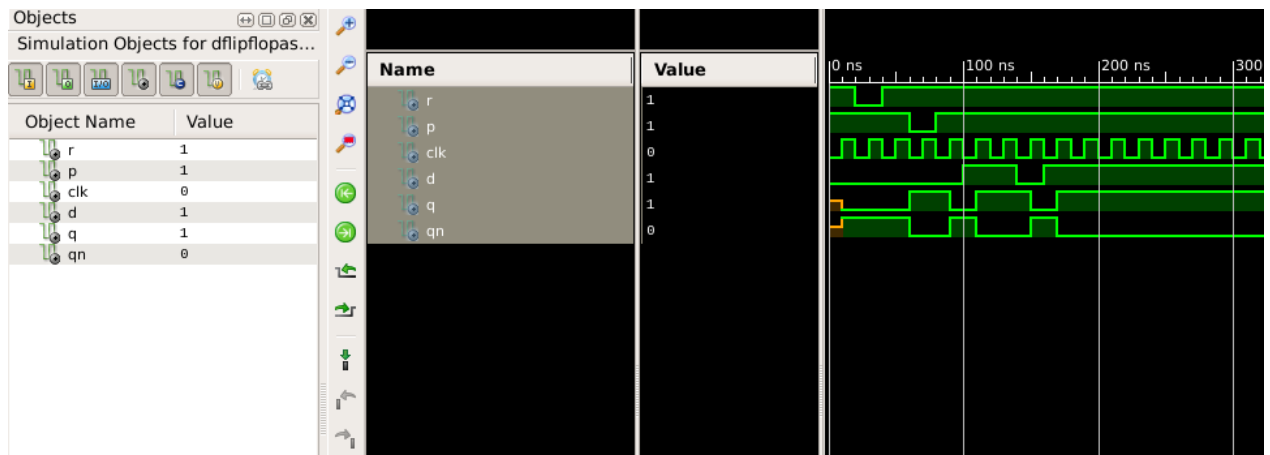

D_Flip_Flop avec Synchrone Enable

```

32 entity DFlipFlopSynchEn is
33     Port ( Rbar : in  STD_LOGIC;
34           Pbar : in  STD_LOGIC;
35           CLk  : in  STD_LOGIC;
36           En   : in  STD_LOGIC;
37           D    : in  STD_LOGIC;
38           Q    : out STD_LOGIC;
39           Qn   : out STD_LOGIC);
40 end DFlipFlopSynchEn;
41
42 architecture Behavioral of DFlipFlopSynchEn is
43
44 begin
45     process (Rbar, Pbar, Clk)
46     begin
47         if Rbar = '0' then
48             Q <= '0';
49             Qn <= '1';
50         elsif Pbar = '0' then
51             Q <= '1';
52             Qn <= '0';
53         elsif rising_edge(Clk) then
54             if En = '1' then
55                 Q <= D;
56                 Qn <= not D;
57             end if;
58         end if;
59     end process;
60
61 end Behavioral;
62
63


```


Testbench pour D_Flip_Flop avec Synchrone Enable

```

82      -- Clock process definitions
83      Clk_process :process
84      begin
85          CLk <= '0';
86          wait for CLk_period/2;
87          CLk <= '1';
88          wait for CLk_period/2;
89      end process;
90
91
92      -- Stimulus process
93      stim_proc: process
94      begin
95          Rbar <= '0'; Pbar <= '1'; En <= '1'; D <= '0';
96          wait for clk_period;
97
98          Rbar <= '1'; Pbar <= '0';
99          wait for clk_period;
100
101          Rbar <= '1'; Pbar <= '1'; En <= '0';
102          wait for clk_period;
103
104          En <= '1'; D <= '0';
105          wait for clk_period;
106
107          D <= '1';
108          wait for clk_period;
109
110          wait;
111      end process;
112
113  END;
114

```

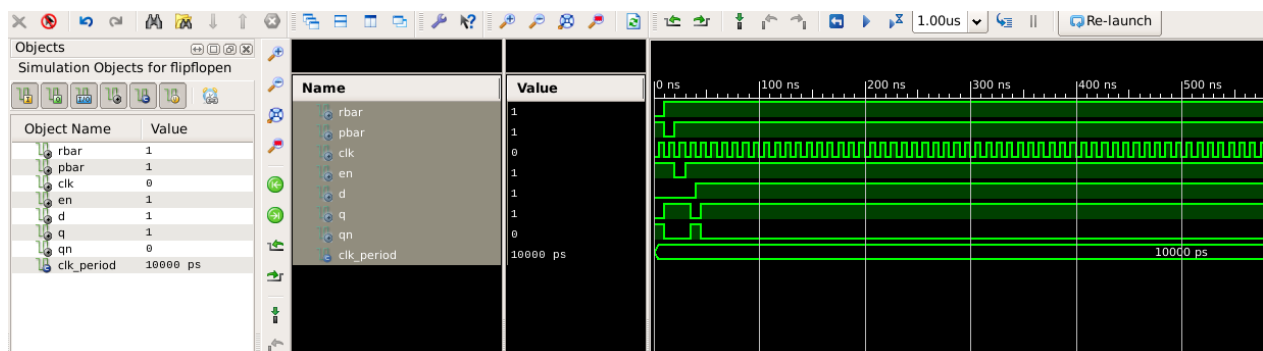

Exercice 2:


1) Register avec Enables 4 bits

Modèle VHDL avec generate

```
31 entity registerEnable is
32   Generic (
33     N : integer := 4
34   );
35   Port (
36     clk      : in  STD_LOGIC;
37     reset    : in  STD_LOGIC;
38     EN       : in  STD_LOGIC;
39     D_in     : in  STD_LOGIC_VECTOR(N-1 downto 0);
40     Q_out    : out STD_LOGIC_VECTOR(N-1 downto 0)
41   );
42 end registerEnable;
43
44 architecture Behavioral of registerEnable is
45   signal reg : STD_LOGIC_VECTOR(N-1 downto 0);
46 begin
47   gen_reg: for i in 0 to N-1 generate
48     process(clk, reset)
49     begin
50       if reset = '0' then
51         reg(i) <= '0';
52       elsif rising_edge(clk) then
53         if EN = '1' then
54           reg(i) <= D_in(i);
55         end if;
56       end if;
57     end process;
58   end generate gen_reg;
59   Q_out <= reg;
60 end Behavioral;
```

Test bench:

```
72
73   clk_process: process
74   begin
75     while true loop
76       clk <= not clk;
77       wait for 10 ns;
78     end loop;
79   end process;
80
81   stim_proc: process
82   begin
83     reset <= '0';
84     wait for 20 ns;
85     reset <= '1';
86
87     wait for 20 ns;
88     EN <= '1';
89     D_in <= "1010";
90     wait for 20 ns;
91
92     en <= '0';
93     D_in <= "1100";
94     wait for 20 ns;
95
96     wait;
97   end process;
98
99 END;
100
```

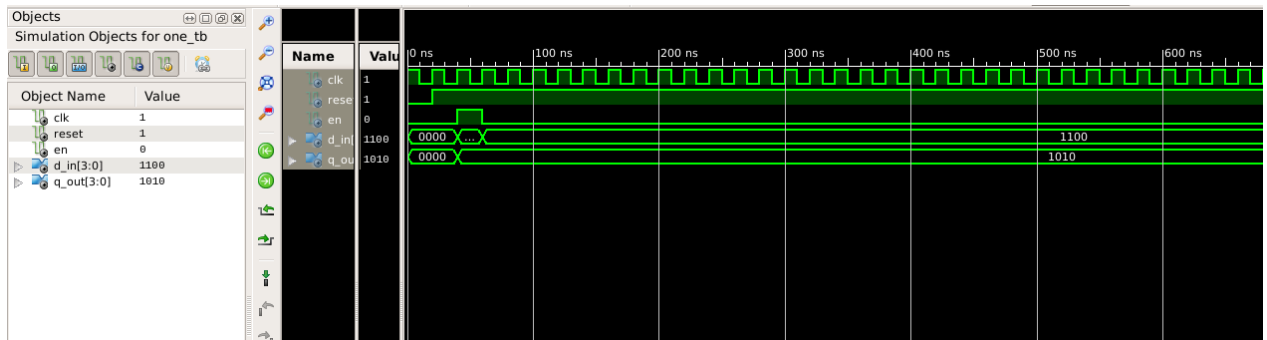

2) Shift Registers:

Modèle VHDL:


```

31
32 entity ShiftRegister is
33     Port ( clk : in  STD_LOGIC;
34           reset : in  STD_LOGIC;
35           Din  : in  STD_LOGIC;
36           Dout : out STD_LOGIC_VECTOR(3 downto 0)
37           );
38 end ShiftRegister;
39
40 architecture Behavioral of ShiftRegister is
41     signal reg : STD_LOGIC_VECTOR(3 downto 0);
42 begin
43     process(clk, reset)
44     begin
45         if reset = '0' then
46             reg <= (others => '0');
47         elsif rising_edge(clk) then
48             reg <= Din & reg(3 downto 1);
49         end if;
50     end process;
51     Dout <= reg;
52 end Behavioral;
53
54

```

Test Bench:

```
71
72     clk_process: process
73     begin
74         while true loop
75             clk <= not clk;
76             wait for 10 ns;
77         end loop;
78     end process;
79
80
81     -- Stimulus process
82     stim_proc: process
83     begin
84         reset <= '0';
85         wait for 20 ns;
86         reset <= '1';
87
88         Din <= '1';
89         wait for 20 ns;
90         Din <= '0';
91         wait for 20 ns;
92         Din <= '1';
93         wait for 20 ns;
94         Din <= '1';
95         wait for 20 ns;
96
97         wait;
98     end process;
99
100     END;
```

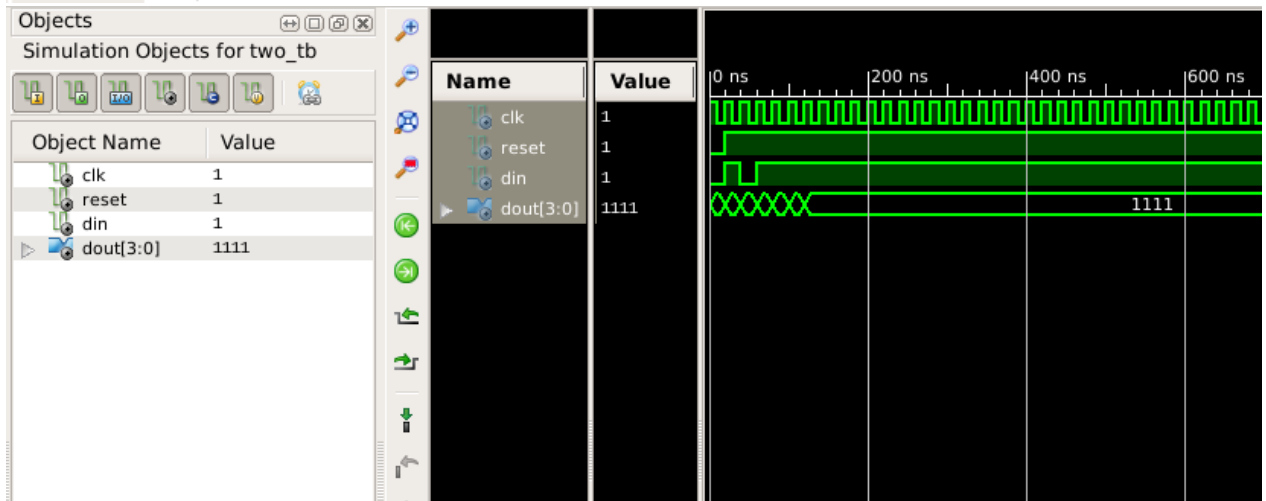

3) Registres sur un Bus de données

Modèle VHDL :

```
32 entity bus_registers is
33     Port ( clk : in  STD_LOGIC;
34           reset : in  STD_LOGIC;
35           A_EN : in  STD_LOGIC;
36           B_EN : in  STD_LOGIC;
37           C_EN : in  STD_LOGIC;
38           Din : in  STD_LOGIC_VECTOR (7 downto 0);
39           A : out  STD_LOGIC_VECTOR (7 downto 0);
40           B : out  STD_LOGIC_VECTOR (7 downto 0);
41           C : out  STD_LOGIC_VECTOR (7 downto 0));
42 end bus_registers;
43
44 architecture Behavioral of bus_registers is
45     signal regA : STD_LOGIC_VECTOR(7 downto 0) := (others => '0');
46     signal regB : STD_LOGIC_VECTOR(7 downto 0) := (others => '0');
47     signal regC : STD_LOGIC_VECTOR(7 downto 0) := (others => '0');
48
49 begin
50     process(clk, reset)
51     begin
52         if reset = '1' then
53             regA <= (others => '0');
54             regB <= (others => '0');
55             regC <= (others => '0');
56         elsif rising_edge(clk) then
57             if A_EN = '1' then
58                 regA <= Din;
59             end if;
60             if B_EN = '1' then
61                 regB <= Din;
62             end if;
63             if C_EN = '1' then
64                 regC <= Din;
65             end if;
66         end if;
67     end process;
68
69     A <= regA;
70     B <= regB;
71     C <= regC;
72
73 end Behavioral;
```

Test Bench :

```

28 LIBRARY ieee;
29 USE ieee.std_logic_1164.ALL;
30
31 -- Uncomment the following library declaration if using
32 -- arithmetic functions with Signed or Unsigned values
33 --USE ieee.numeric_std.ALL;
34
35 ENTITY THREE_TB IS
36 END THREE_TB;
37
38 ARCHITECTURE behavior OF THREE_TB IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT bus_registers
43     PORT (
44         clk : IN  std_logic;
45         reset : IN  std_logic;
46         A_EN : IN  std_logic;
47         B_EN : IN  std_logic;
48         C_EN : IN  std_logic;
49         Din : IN  std_logic_vector(7 downto 0);
50         A : OUT  std_logic_vector(7 downto 0);
51         B : OUT  std_logic_vector(7 downto 0);
52         C : OUT  std_logic_vector(7 downto 0)
53     );
54     END COMPONENT;
55
56 --Inputs
57 signal clk : std_logic := '0';
58 signal reset : std_logic := '0';
59 signal A_EN : std_logic := '0';
60 signal B_EN : std_logic := '0';
61 signal C_EN : std_logic := '0';
62 signal Din : std_logic_vector(7 downto 0) := (others => '0');
63
64 --Outputs
65 signal A : std_logic_vector(7 downto 0);
66 signal B : std_logic_vector(7 downto 0);
67 signal C : std_logic_vector(7 downto 0);
68
69 BEGIN
70
71     -- Instantiate the Unit Under Test (UUT)
72     uut: bus_registers PORT MAP (
73         clk => clk,
74         reset => reset,
75         A_EN => A_EN,
76         B_EN => B_EN,
77         C_EN => C_EN,
78         Din => Din,
79         A => A,
80         B => B,
81         C => C
82     );
83
84
85

```

```

85
86     clk_process: process
87     begin
88         while true loop
89             clk <= not clk;
90             wait for 10 ns;
91         end loop;
92     end process;
93
94     -- Stimulus process
95     stim_proc: process
96     begin
97         reset <= '1';
98         wait for 20 ns;
99         reset <= '0';
100
101         Din <= "10101010"; A_EN <= '1'; wait for 20 ns;
102         A_EN <= '0';
103         Din <= "11001100"; B_EN <= '1'; wait for 20 ns;
104         B_EN <= '0';
105         Din <= "11110000"; C_EN <= '1'; wait for 20 ns;
106         C_EN <= '0';
107         wait;
108     end process;
109
110 END;

```

